

Part 1: Diodes	1	Part 2: Transistors	183
Introduction to Diode.....	2	SCRs(c) Thyristors.....	183
Transformers & Filters (Power supply circuit).....	10	Shockley Diode.....	184
Diode Limiters, clampers & Voltage Multipliers.....	19	Silicon-controlled rectifier (SCR).....	189
The Zener Diode.....	30	How to control the power of SCR.....	194
Varactor Diode and Light Emitting Diode (LED).....	40	About Diac.....	200
Photo Diode and Laser Diode.....	49	About Triac.....	204
Schottky, PIN, Tunnel Diode & Current Regulator Diode.....	57	Triac Phase Control.....	212
 		SCS, UJT and PUT.....	219
Part 3: Bipolar Junction Transistor	63	 	
Introduction to Bipolar Junction Transistor.....	64	Part 4: Operational Amplifier	225
Bipolar Junction Transistor Electrons Flow.....	68	Differential Amplifier.....	226
BJT as a switch and Reading Datasheet.....	73	Negative feedback.....	232
Coupling Capacitor and Bypassing Capacitor.....	81	Comparator.....	240
BJT as an Amplifier (About the Signal).....	86	Summing Amplifiers.....	246
BJT as an Amplifier-2 (Amplifier Classes).....	91	Op-amp Integrator.....	254
BJT as an Amplifier-3 (Class-B amplifier).....	98	Op-amp Differentiator.....	259
BJT as an Amplifier-4 (Class-AB amplifier).....	103	Hysteresis & Output Bounding.....	262
BJT as an Amplifier-5 (Class-C amplifier and Resonant circuit).....	109	Op-amp applications.....	268
Darlington pair and Sziklai pair.....	116	 	
Phototransistor and Photodiode.....	122	Part 5: Filter	275
How to Measure a BJT Transistor.....	127	Capacitive Reactance.....	276
 		What Is Decibel?.....	280
Part 6: Field Effect Transistor	132	Passive Low Pass Filter.....	284
Introduction to Field Effect Transistor.....	133	Passive High Pass Filter & Second Order filters.....	290
Junction Field Effect Transistor.....	138	Passive Band Pass Filter.....	296
Junction Field Effect Transistor - 2.....	144	Active Low Pass Filter.....	301
Metal Oxide Semiconductor Field Effect Transistor (MOSFET).....	148	Active High Pass Filter.....	307
MOSFET as a Switch.....	152	Active Band Pass Filter.....	314
MOSFET as a Switch-2.....	156	Active Band Stop Filter.....	321
H-Bridge motor control with MOSFET.....	162	Active filter ප්‍රකාශනය සැපයීම් Transfer function.....	329
Other Types of MOSFET.....	166	 	
Insulated-gate bipolar transistor (IGBT).....	171		
Testing Field Effect Transistors.....	176		